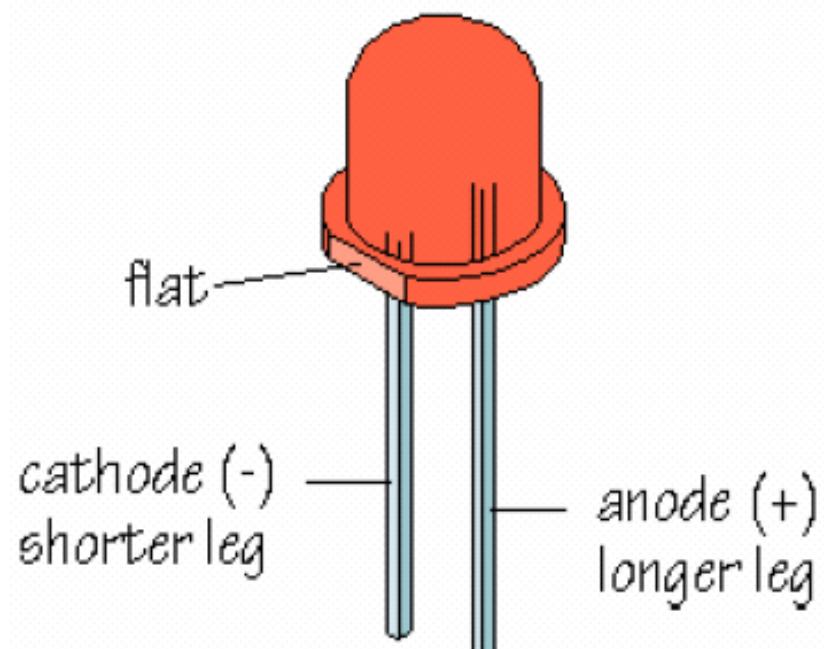



Light Emitting Diode: LED

What is an LED?

- Light-emitting diode
- Semiconductor
- Has polarity




1) How It Works

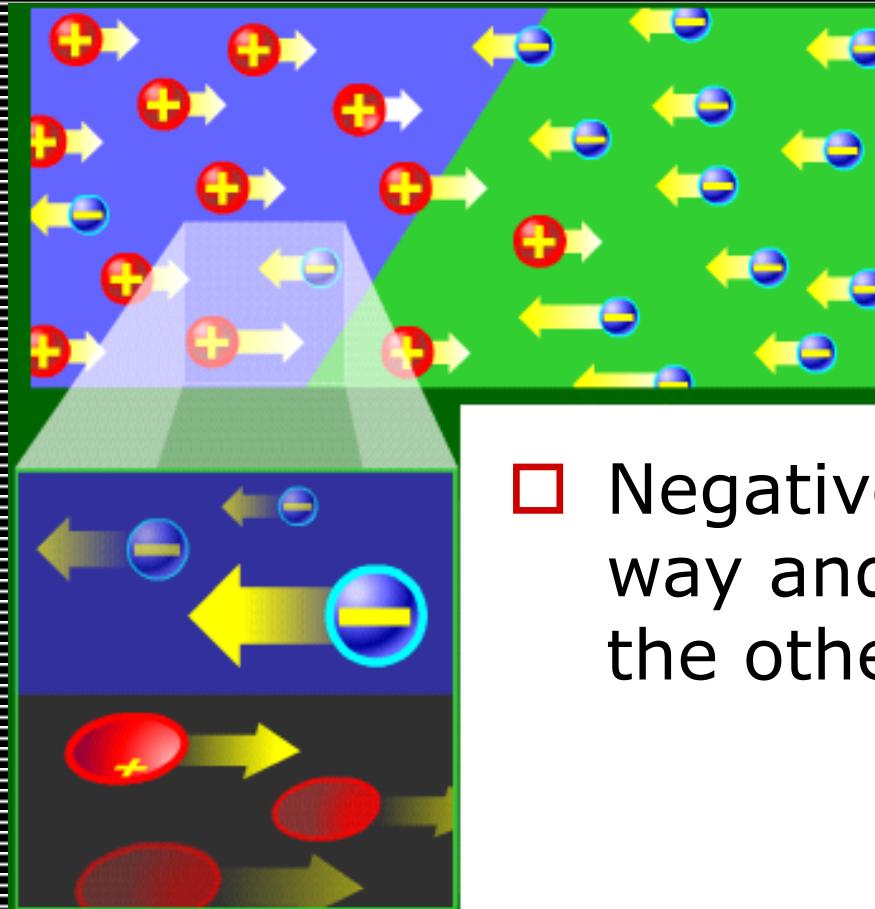


- When current flows across a diode
- Negative electrons move one way and positive holes move the other way

LED: How It Works

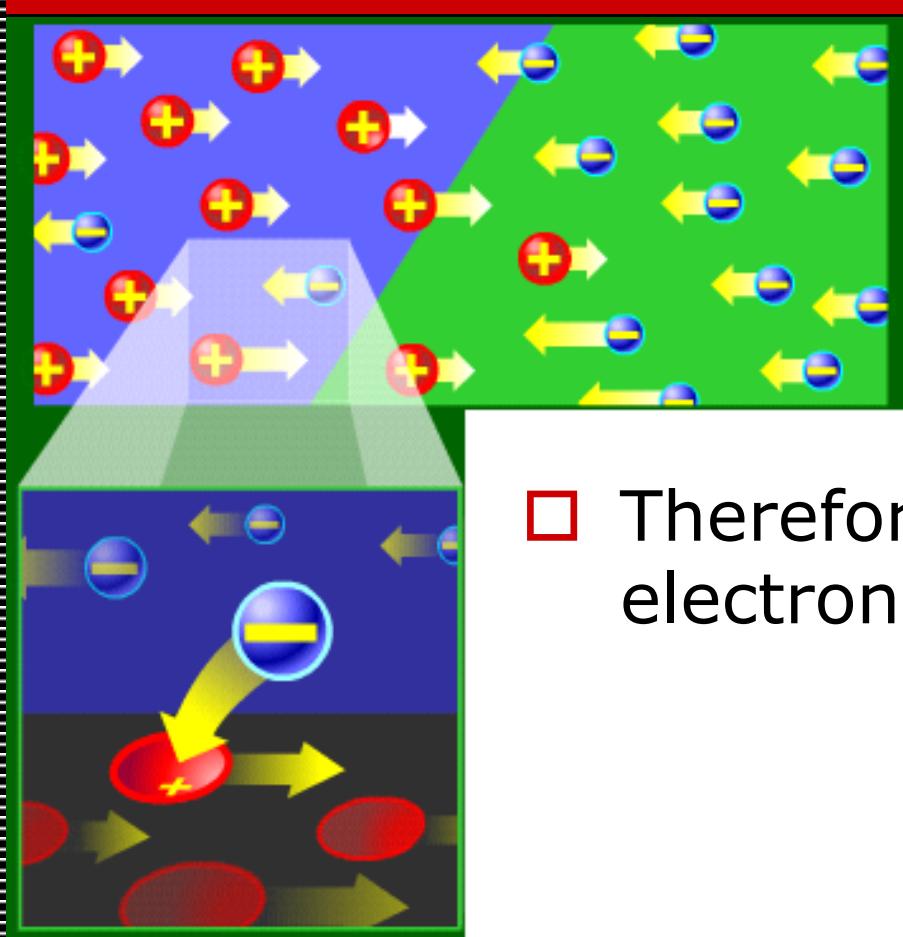


- The holes exist at a lower energy level than the free electrons
- Therefore when a free electrons falls it losses energy

1) How It Works

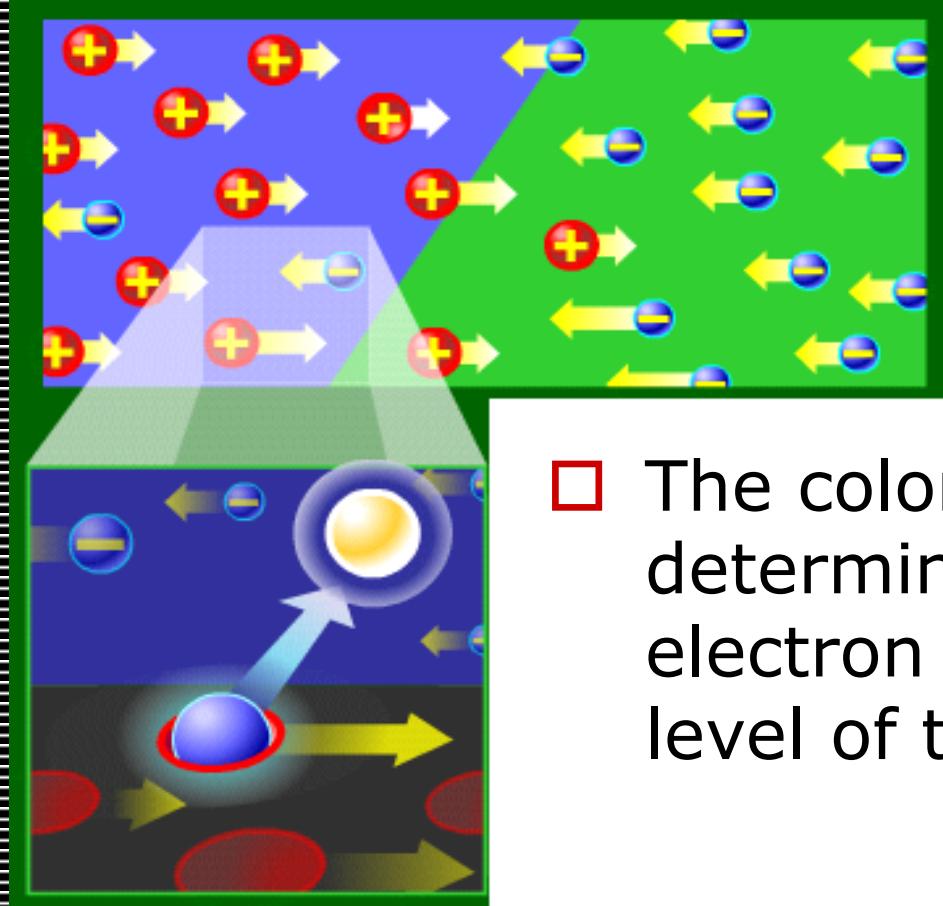


- This energy is emitted in a form of a photon, which causes light
- The color of the light is determined by the fall of the electron and hence energy level of the photon

Inside a Light Emitting Diode

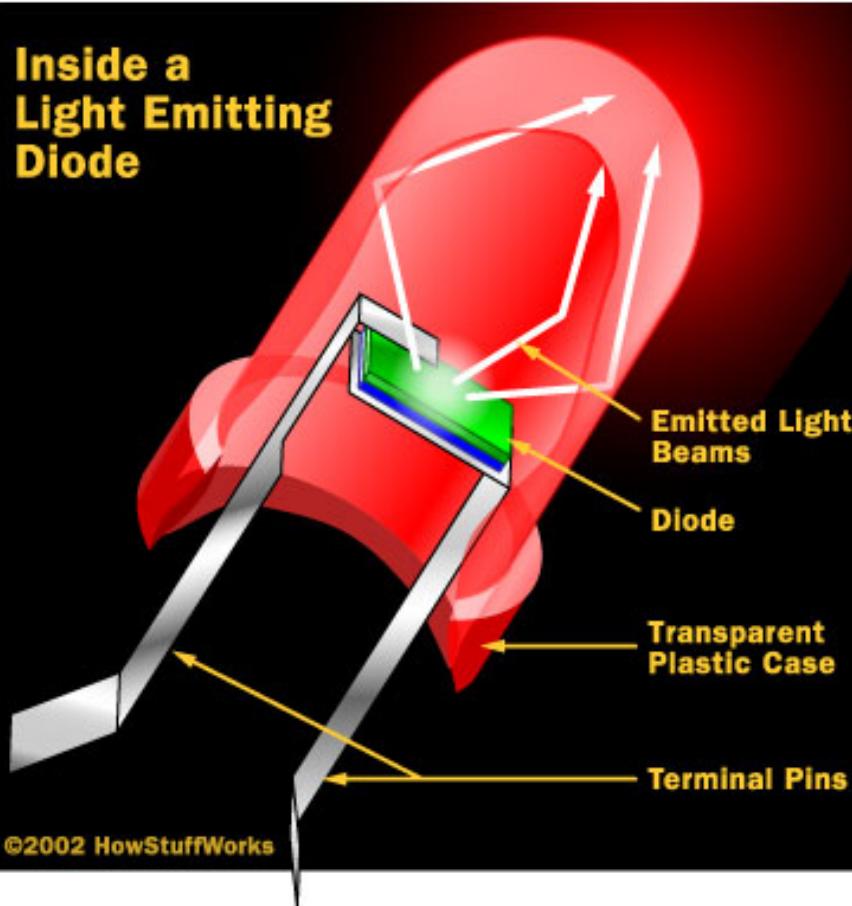


1. transparent Plastic Case
2. terminal Pins
3. Diode

Kinds of LEDs

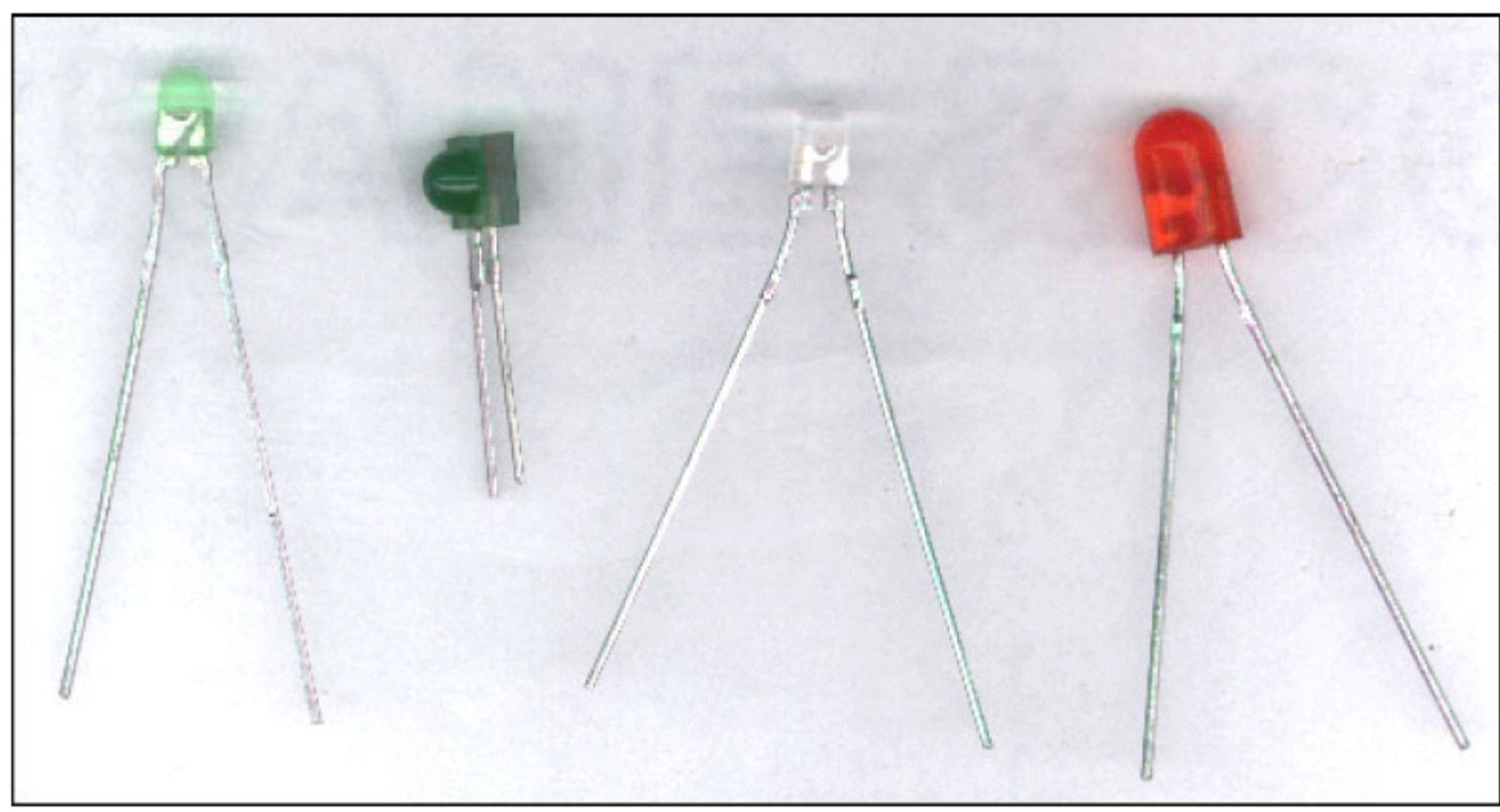


How to Connect a LED:

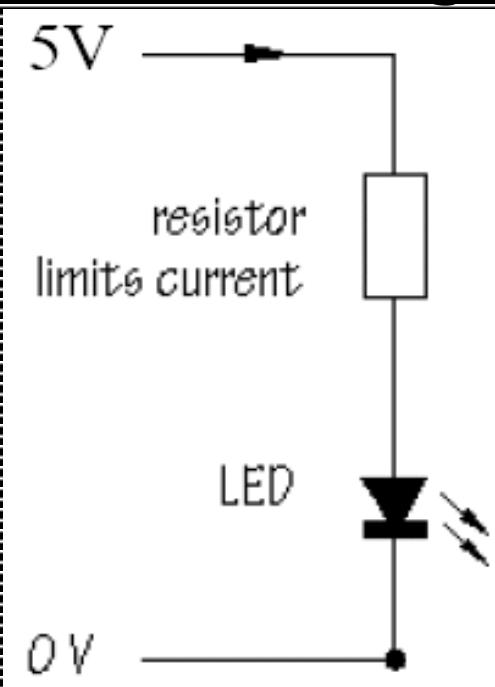- Requires 1.5~2.5V and 10 mA
- To prevent overloading, use resistor 470 Ω




How to Connect a LED;

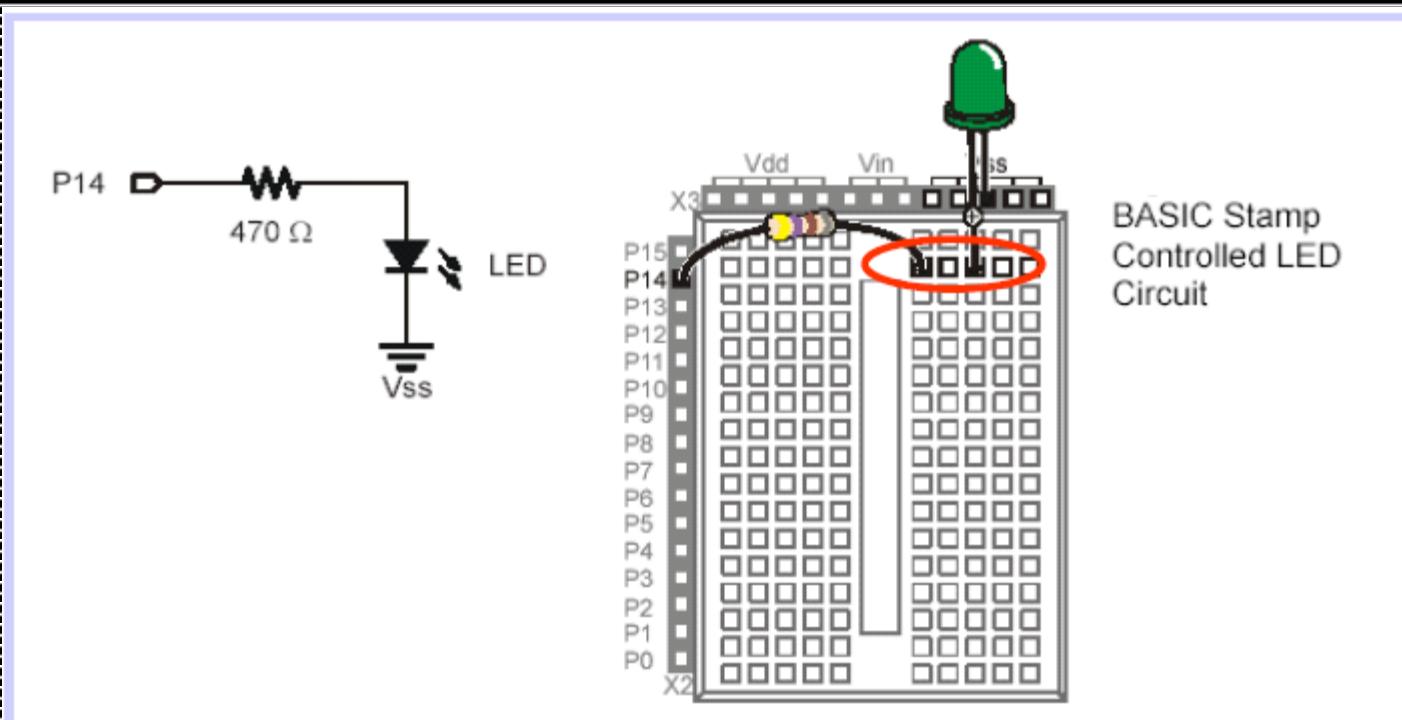


Connect LED to BS12

- LED is on when P0 is high

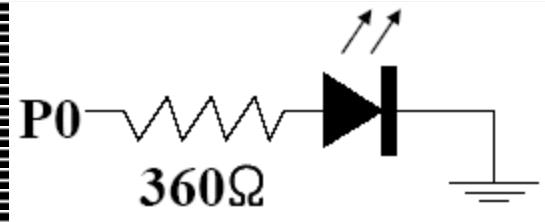


- LED is on when P1 is low

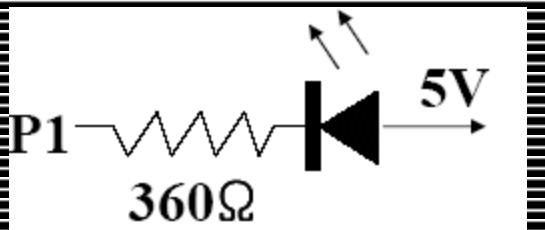




Connect Multiple LEDs to BS2

- 8 LEDs are connected to BS2 each I/O pin (P0-P7) is allowed to sink 6.25mA
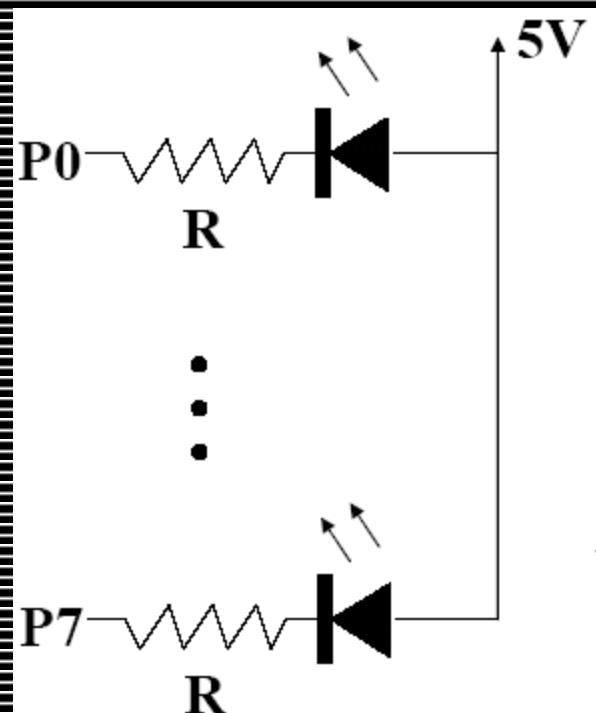
$$R = \frac{V}{I} = \frac{3.6}{6.25 \times 10^{-3}} = 576\Omega$$



Case Study: Blinking LED

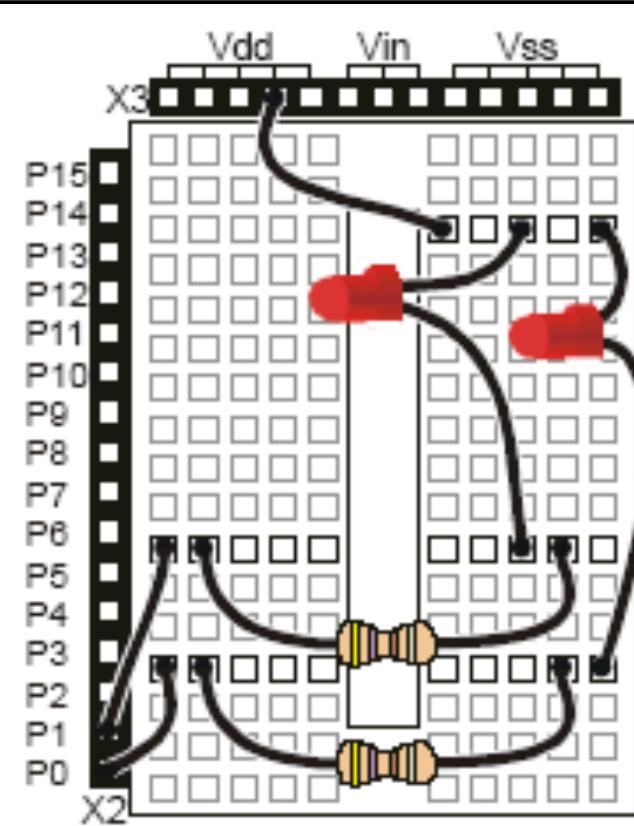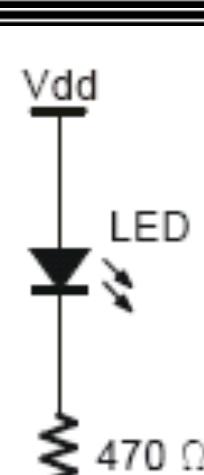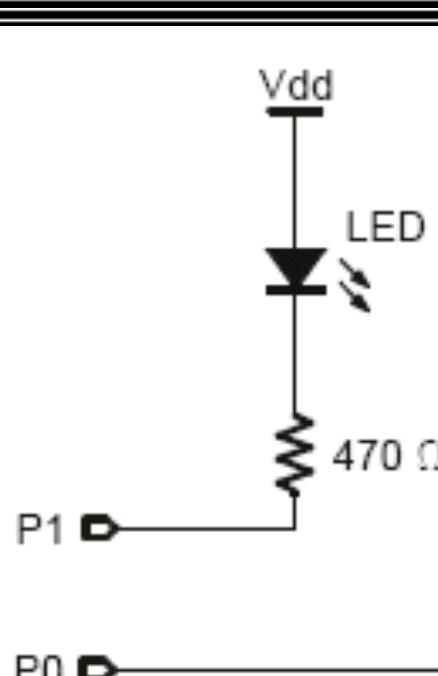

Case Study: Blinking LED

☐ Pbasic program to make an LED blink

output 0	→ Make pin0 an output
Main:	→ Loop begins here
low 0	→ Turn LED on
pause 1000	→ Pause for 1 sec
high 0	→ Turn LED off
pause 1000	→ Pause for 1 sec
goto Main	→ Go back to beginning of loop

Experiments

- Flash an LED
 - 1. Single LED
 - 2. Multiple LEDs
- Traffic Light by use of LEDs
